

CS2100

TUTORIAL #5

MIPS PROCESSOR: DATAPATH AND CONTROL

(PREPARED BY: AARON TAN)

From
lecture
slide:

Generating ALUControl Signal

Opcode	ALUop	Instruction Operation	Funct field	ALU action	ALU control
lw	00	load word	xxxxxx	add	0010
sw	00	store word	xxxxxx	add	0010
beq	01	branch equal	xxxxxx	subtract	0110
R-type	10	add	10 0000	add	0010
R-type	10	subtract	10 0010	subtract	0110
R-type	10	AND	10 0100	AND	0000
R-type	10	OR	10 0101	OR	0001
R-type	10	set on less than	10 1010	set on less than	0111

Instruction Type	ALUop
lw / sw	00
beq	01
R-type	10

ALUcontrol	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	slt
1100	NOR

Generation of 2-bit **ALUop** signal will be discussed later

From
lecture
slide:

Design of ALU Control Unit (1/2)

- **Input:** 6-bit **Func** field and 2-bit **ALUop**
- **Output:** 4-bit **ALUcontrol**
- Find the simplified expressions

ALUcontrol3 = 0

ALUcontrol2 = ?


$\text{ALUop0} + \text{ALUop1} \cdot \text{F1}$

	ALUop		Func Field (F[5:0] == Inst[5:0])						ALU control
	MSB	LSB	F5	F4	F3	F2	F1	F0	
lw	0	0	X	X	X	X	X	X	0 0 1 0
sw	0	0	X	X	X	X	X	X	0 0 1 0
beq	0 X	1	X	X	X	X	X	X	0 1 1 0
add	1	0 X	1 X	0 X	0	0	0	0	0 0 1 0
sub	1	0 X	1 X	0 X	0	0	1	0	0 1 1 0
and	1	0 X	1 X	0 X	0	1	0	0	0 0 0 0
or	1	0 X	1 X	0 X	0	1	0	1	0 0 0 1
slt	1	0 X	1 X	0 X	1	0	1	0	0 1 1 1

From
lecture
slide:

Control Design: Outputs

	RegDst	ALUSrc	MemTo Reg	Reg Write	Mem Read	Mem Write	Branch	ALUop	
								op1	op0
R-type	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

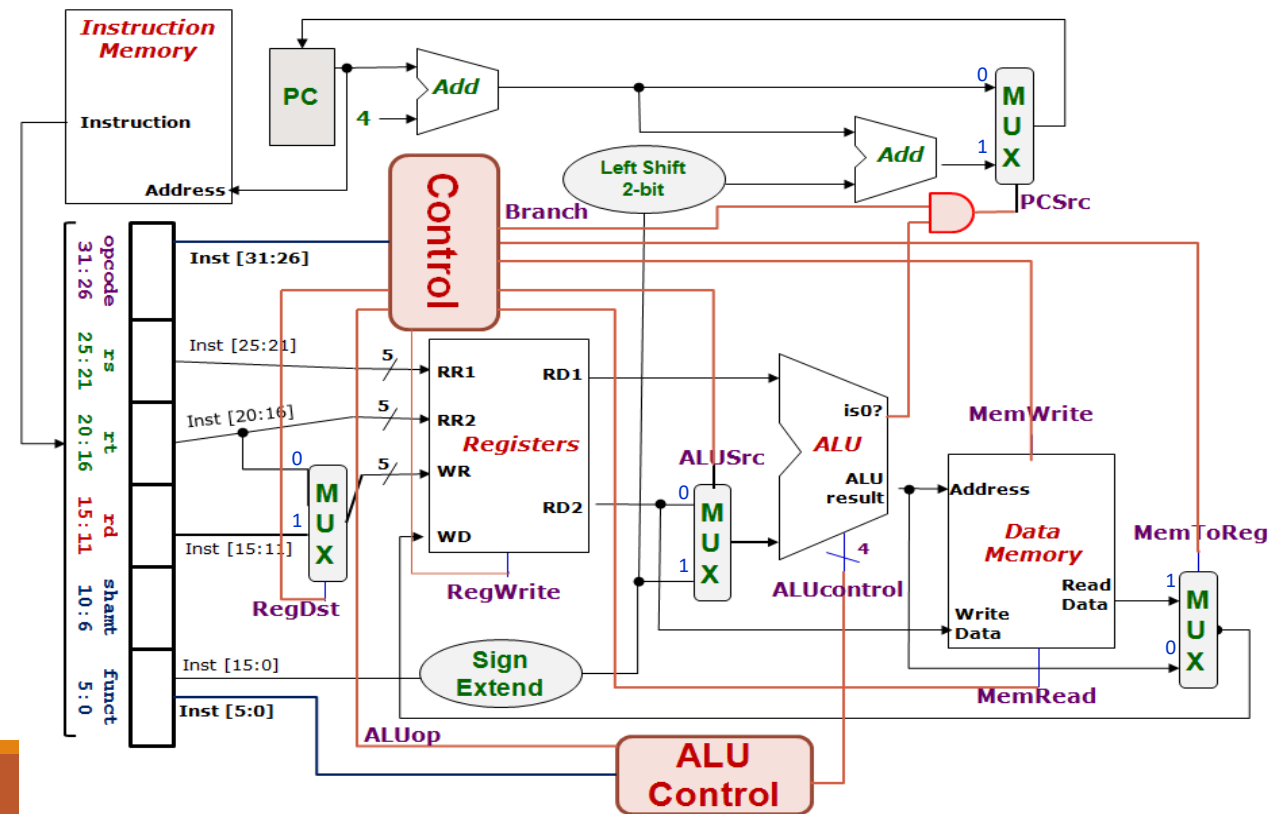


beq \$1, \$3, 12

If (R[rs]==R[rt]) PC=PC+4+BrAddr

000100 00001 00011 0000000000001100

Q1(ii)

Registers File				ALU		Data Memory	
RR1	RR2	WR	WD	Opr1	Opr2	Address	Write Data
\$1	\$3	\$3 or \$0	[\$1]-[\$3] or random value	[\$1]	[\$3]	[\$1] - [\$3]	[\$3]

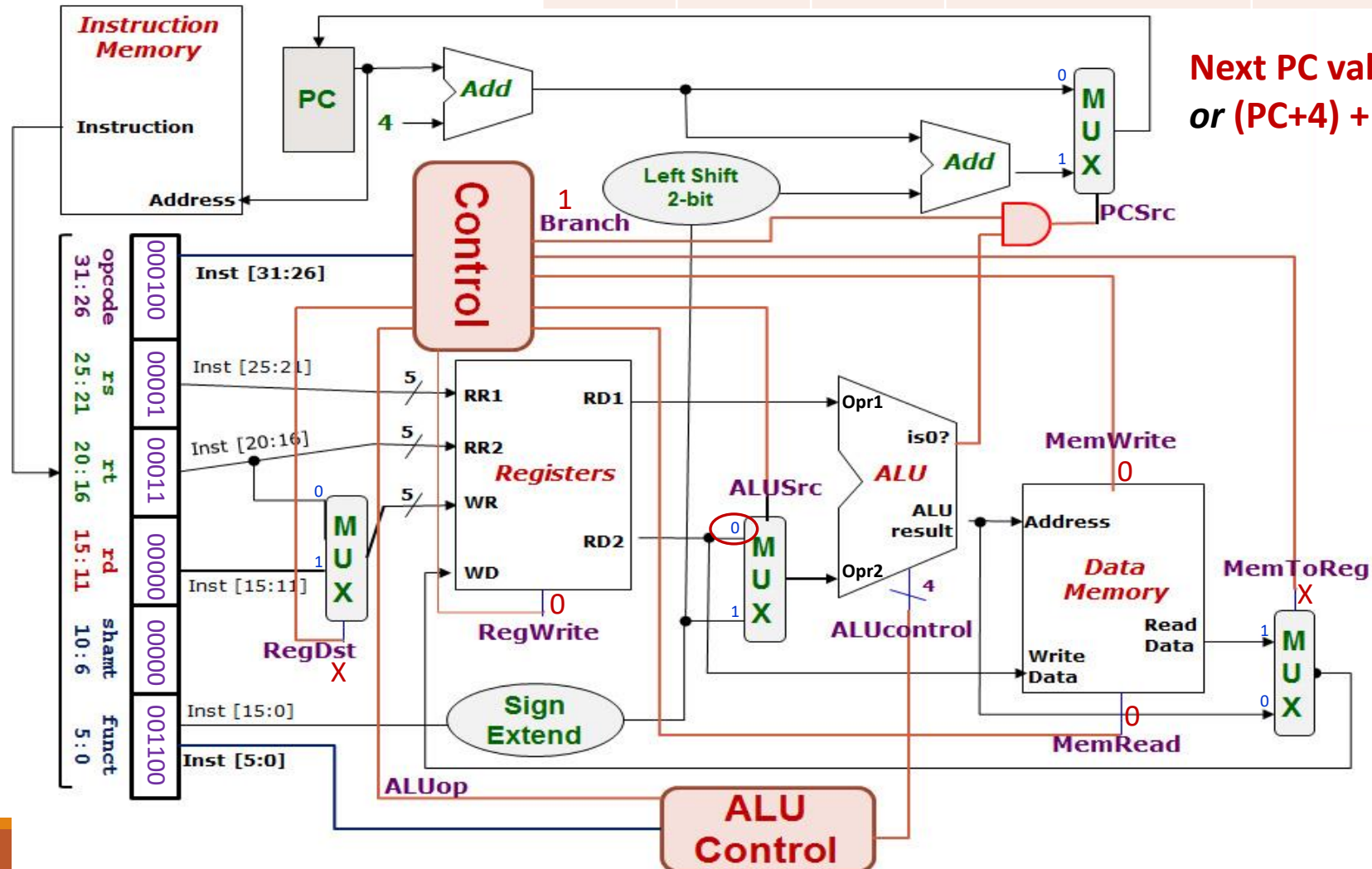

RegDest	X
RegWrite	0
ALUSrc	0
MemRead	0
MemWrite	0
MemToReg	X
Branch	1
ALUop	01
ALUcontrol	0110


sub \$25, \$20, \$5

$R[rd] = R[rs] - R[rt]$

000000 10100 00101 11001 00000 100010

Q1(iii)

Registers File				ALU		Data Memory	
RR1	RR2	WR	WD	Opr1	Opr2	Address	Write Data
\$20	\$5	\$25	$[\$20] - [\$5]$	$[\$20]$	$[\$5]$	$[\$20] - [\$5]$	$[\$5]$

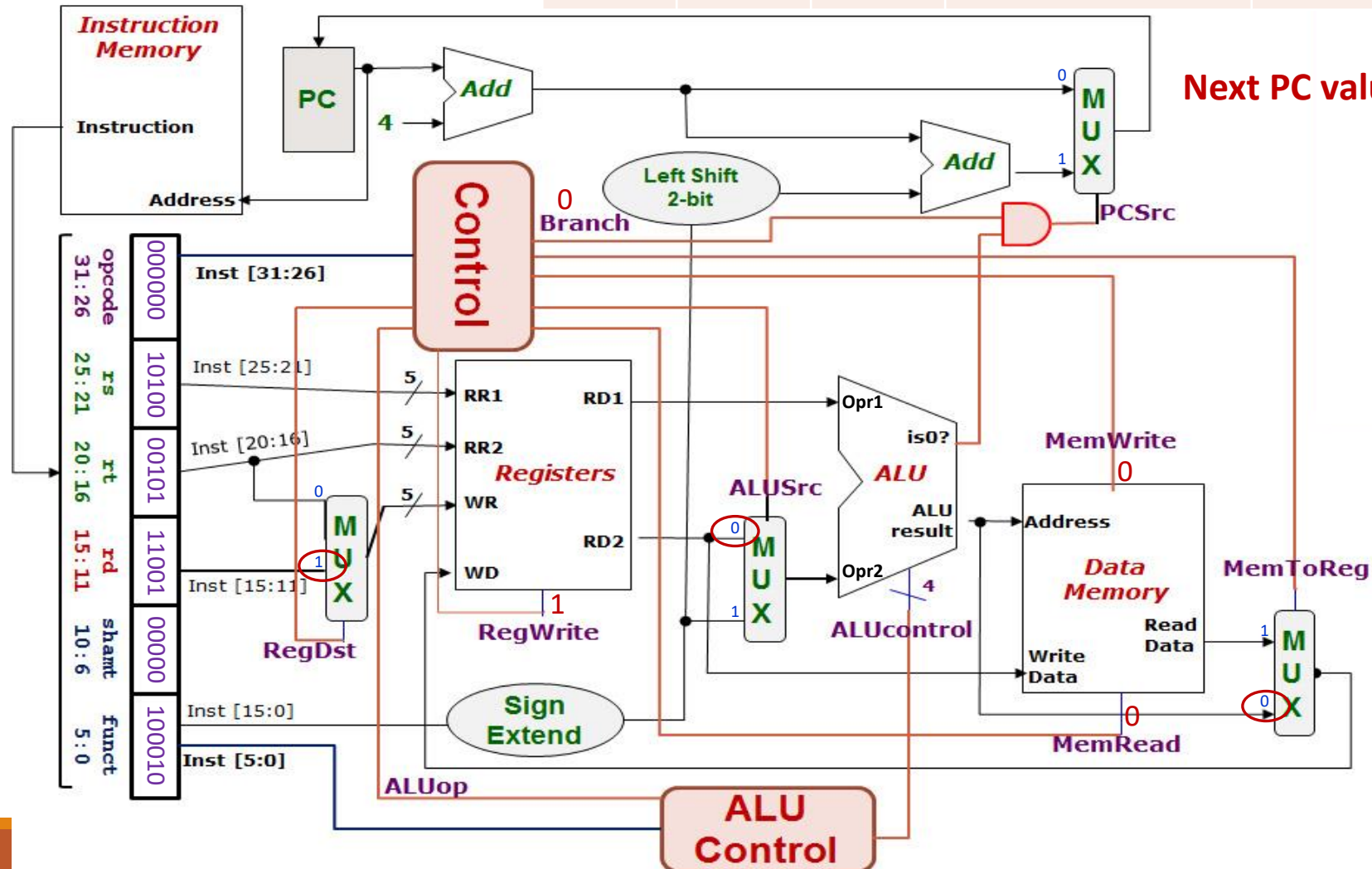


RegDest	1
RegWrite	1
ALUSrc	0
MemRead	0
MemWrite	0
MemToReg	0
Branch	0
ALUOp	10
ALUcontrol	0110

Critical Path Analysis




Duration = $a + b + c$

Sequence/Series

 

Duration = $\max(a, b, c)$

Parallel

 

Critical path duration = $5 + 4 + 8 + 6 = 23$

SUB instruction

Inst-Mem (400) → Reg.File (200) → MUX (ALUSrc) (30) → ALU (120) → MUX (MToR) (30) → Reg.File (200)

Control (100) *Not critical path*

Q2(a)

Inst-Mem
400ps

Adder
100ps

MUX
30ps

ALU
120ps


Reg-File
200ps

Data-Mem
350ps

Control/ALU
Control
100ps

Lshft/signext
/AND
20ps
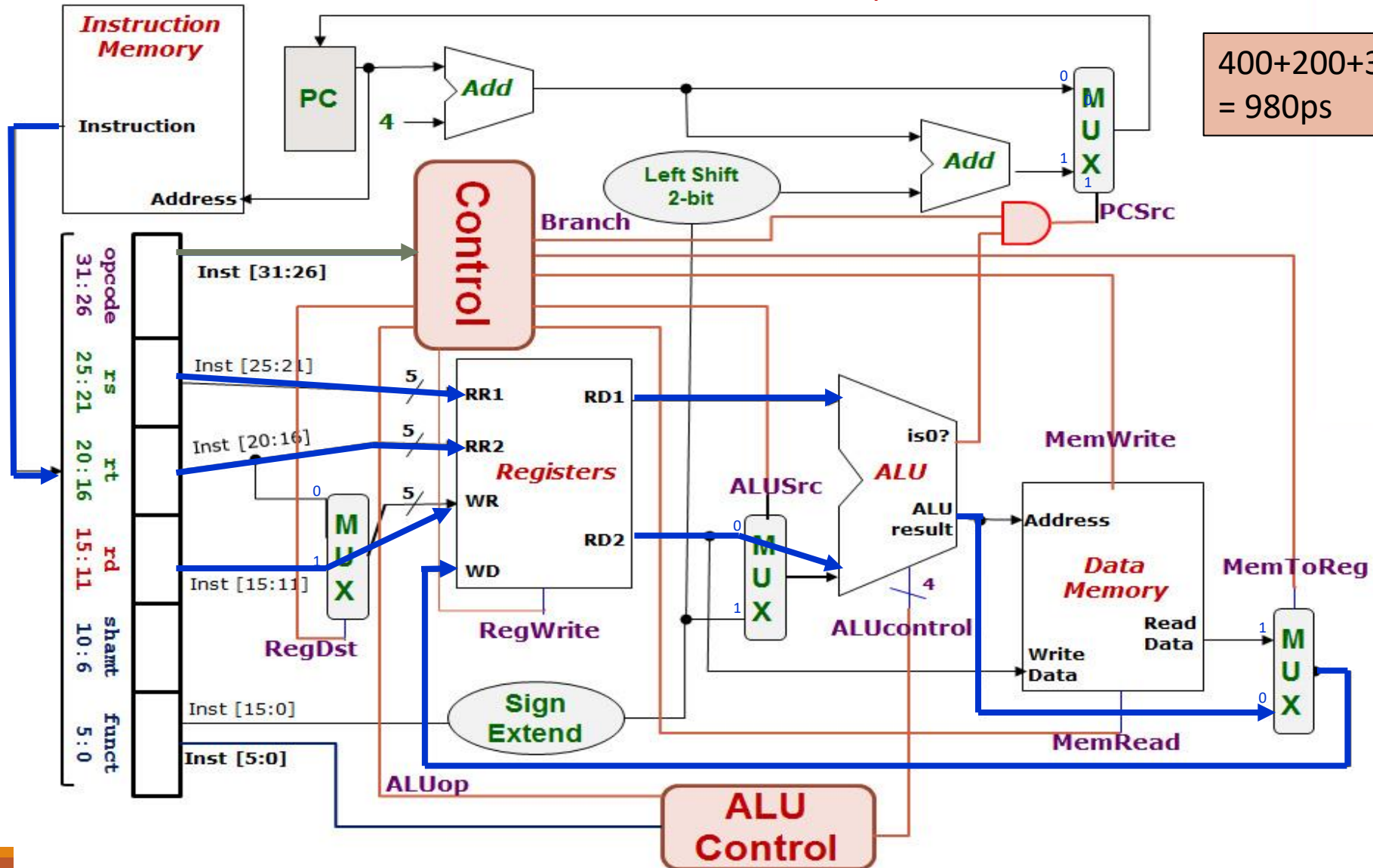
$$400 + 200 + 30 + 120 + 30 + 200 = 980\text{ps}$$



LW instruction

Inst-Mem (400) → Reg.File (200) → ALU (120) → DataMem (350) → MUX (MToR) (30) → Reg.File (200)

Control (100) *Not critical path*

Q2(b)

Inst-Mem
400ps

Adder
100ps

MUX
30ps

ALU
120ps


Reg-File
200ps

Data-Mem
350ps

Control/ALU
Control
100ps

Lshft/signext
/AND
20ps
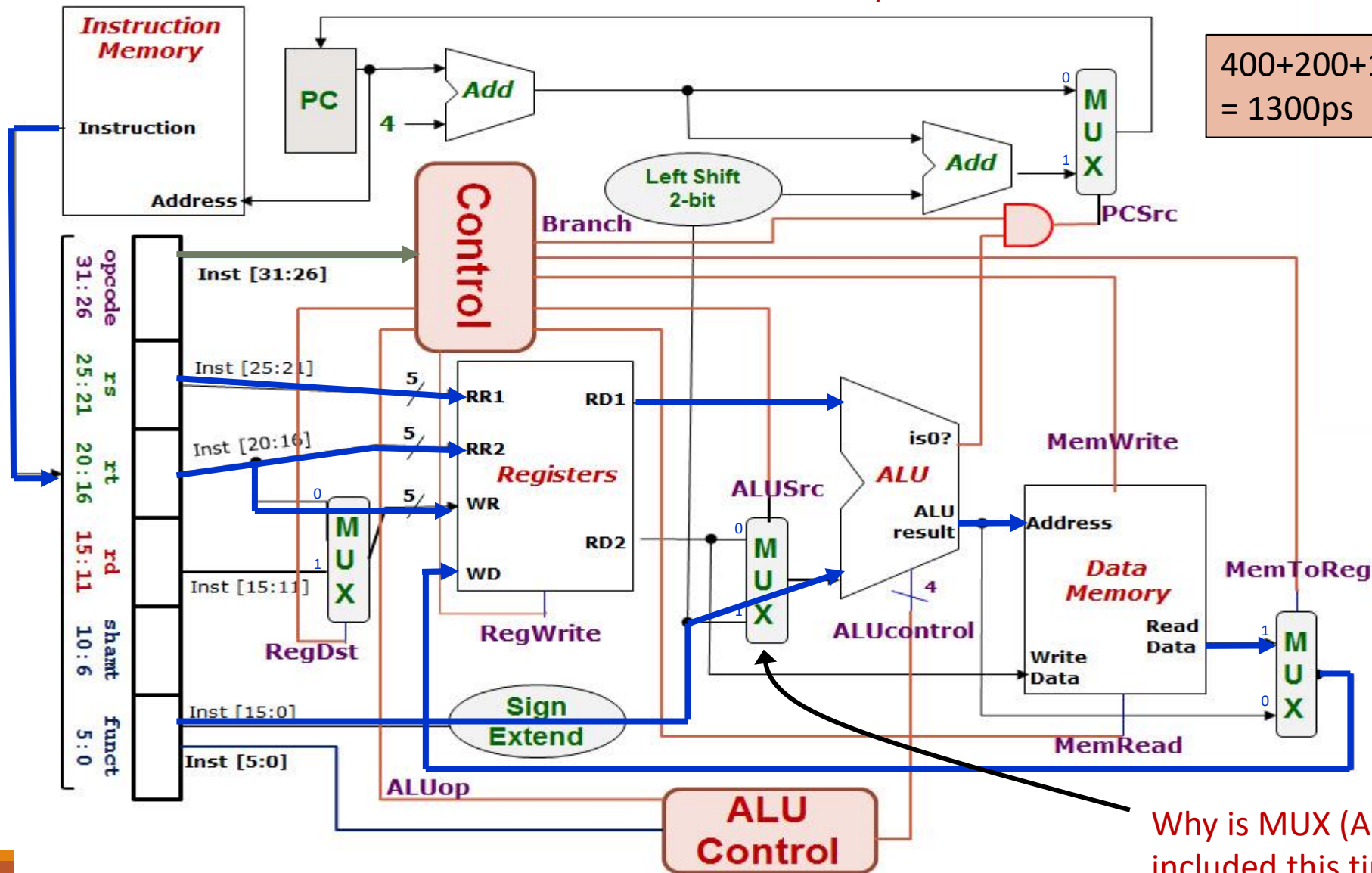
$$400 + 200 + 120 + 350 + 30 + 200 = 1300\text{ps}$$



Why is MUX (ALUSrc) not included this time?

BEQ instruction

Inst-Mem (400) → Reg.File (200) → MUX (ALUSrc) (30) → ALU (120) → AND (20) → MUX (PCSrc) (30)

Control (100) *Not critical path*

Q2(c)

Inst-Mem
400ps

Adder
100ps

MUX
30ps


ALU
120ps

Reg-File
200ps

Data-Mem
350ps

Control/ALU
Control
100ps


Lshft/signext
/AND
20ps

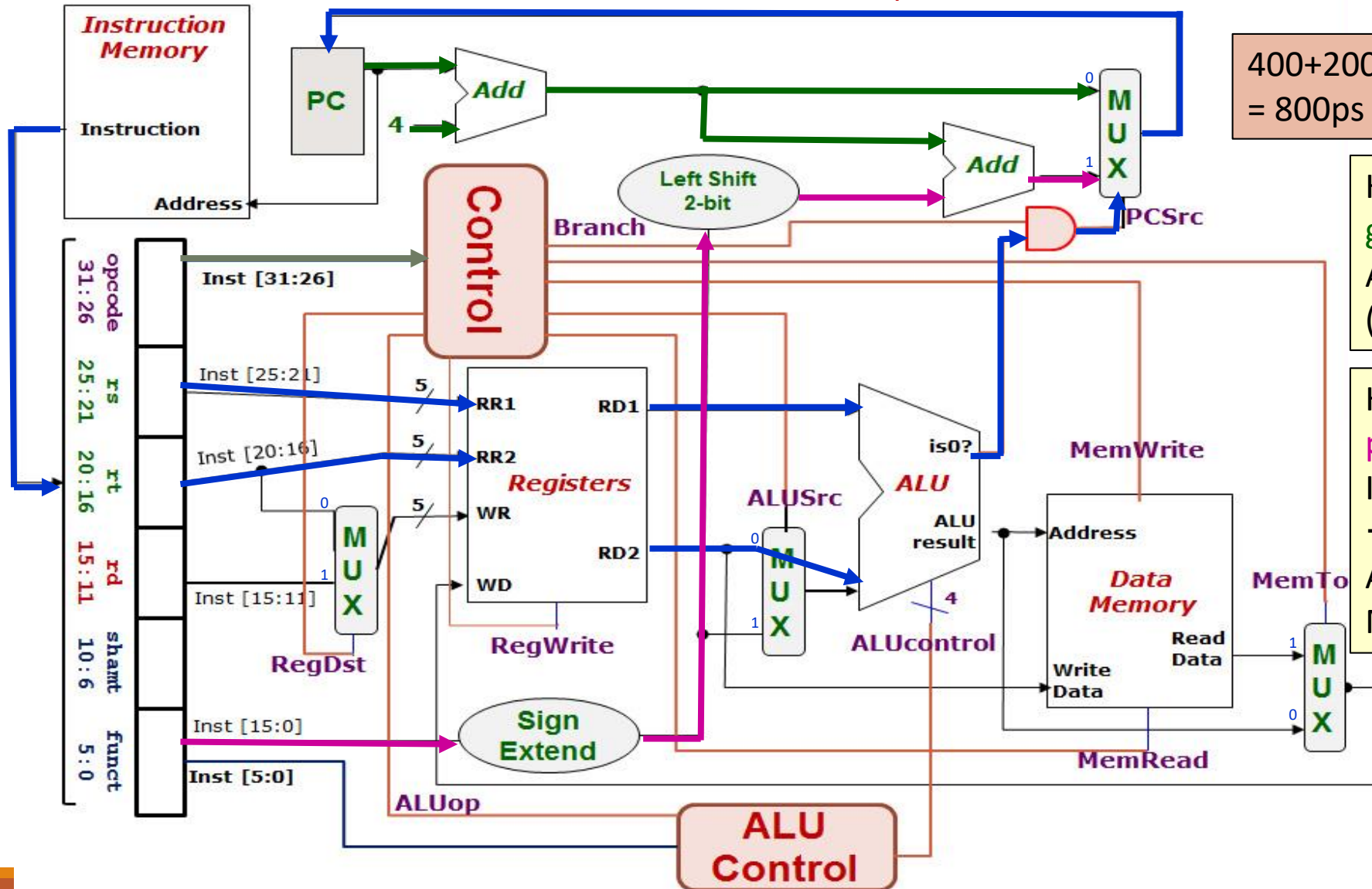

$$400+200+30+120+20+30 = 800ps$$

How about the green path: PC → Adder → MUX (PCSrc)?

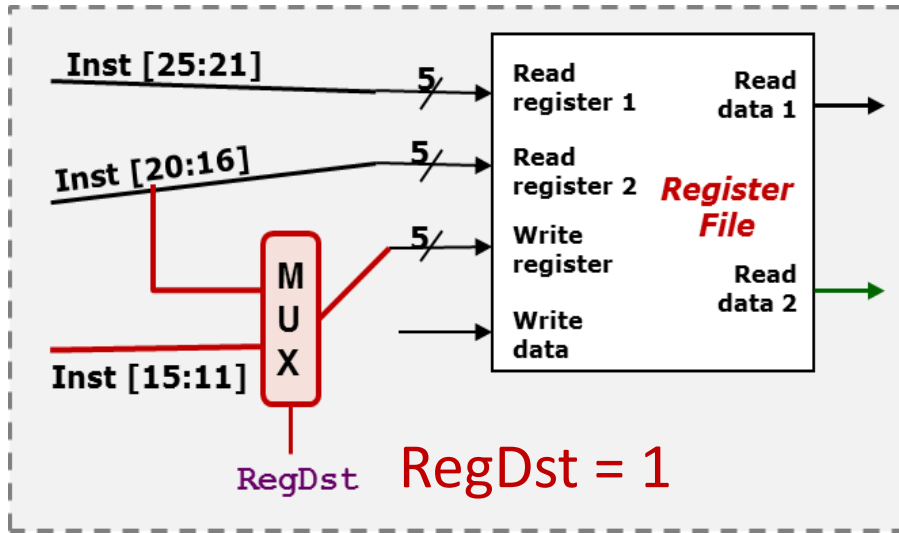How about the purple path: Inst.Mem → SignExt → LeftShift → Adder → MUX(PCSrc)?



Q3(a) add instruction

- (i) One example where the incorrect processor still gives the **right** execution result.

Many possible answers.


Make RT = RD.

Example: **add \$t0, \$t1, \$t0**

- (ii) One example where the incorrect processor gives the **wrong** execution result.


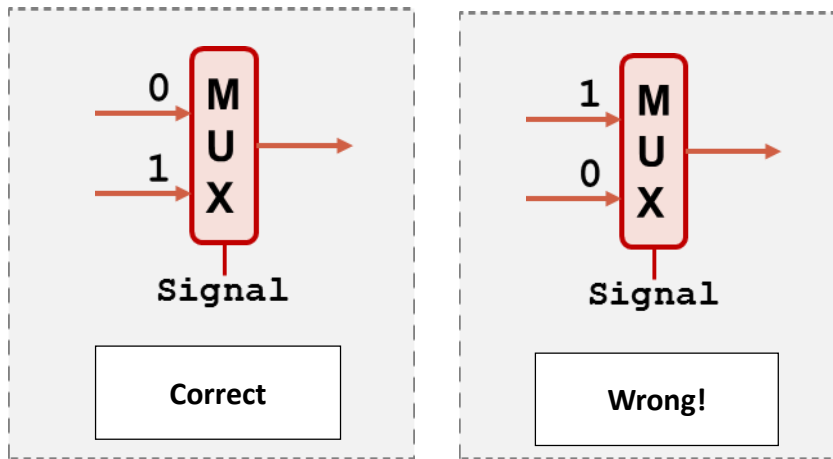
Example: **add \$t0, \$t1, \$t2**

\$t2 instead of \$t0 is picked as write register.



$$R[rd] = R[rs] + R[rt]$$

opcode	rs	rt	rd	shamt	funct
--------	----	----	----	-------	-------

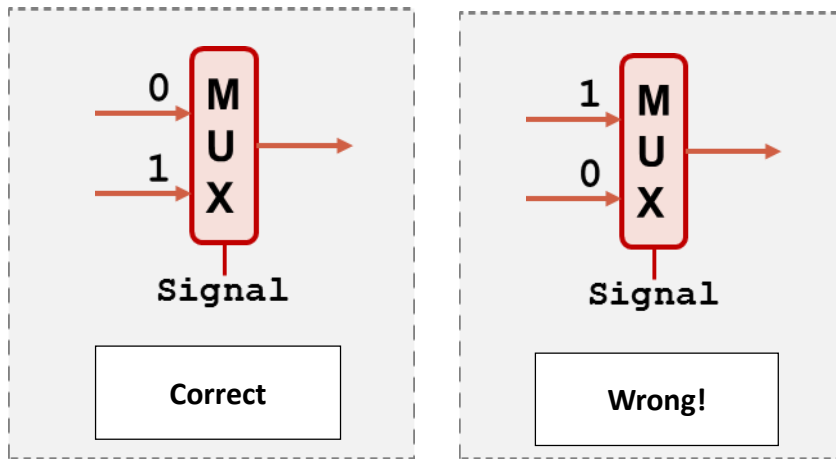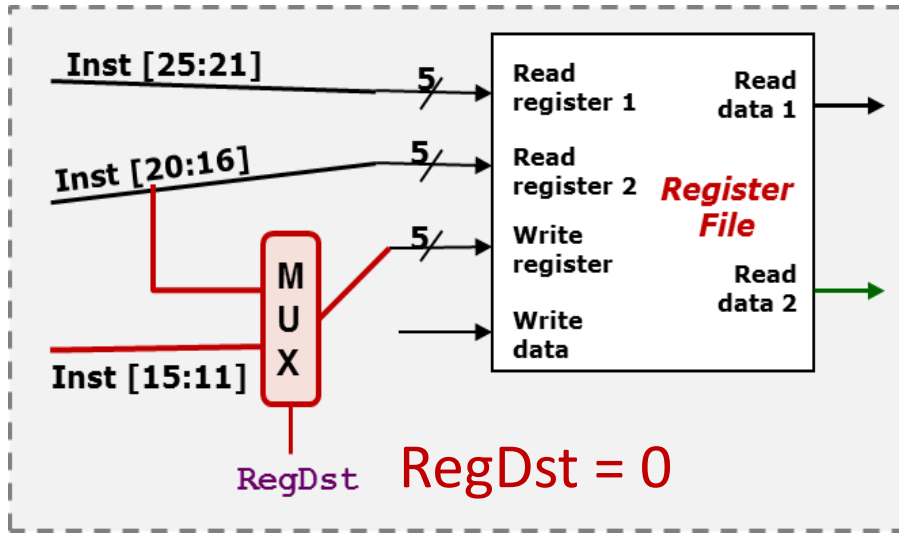

$$R[rt] = M[R[rs] + \text{SignExtImm}]$$

opcode	rs	rt	immed
--------	----	----	-------


Q3(b) lw instruction

- (i) One example where the incorrect processor still gives the **right** execution result.

Make the first 5 bits of immediate value the same as the register number of RT.


Example: **lw \$a0, 8192(\$t0)**

8192 = 0x2000

 

- (ii) One example where the incorrect processor gives the **wrong** execution result.

Anything other than (i).

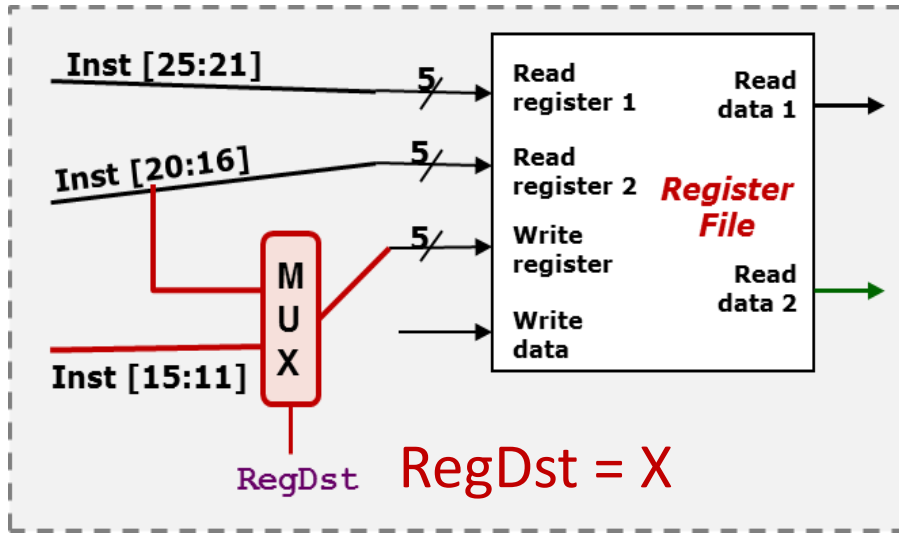



Q3(c) beq instruction

- (i) One example where the incorrect processor still gives the **right** execution result.


Anything will work, since error has no impact on branch instructions.

- (ii) One example where the incorrect processor gives the **wrong** execution result.

None.

  

For your use.

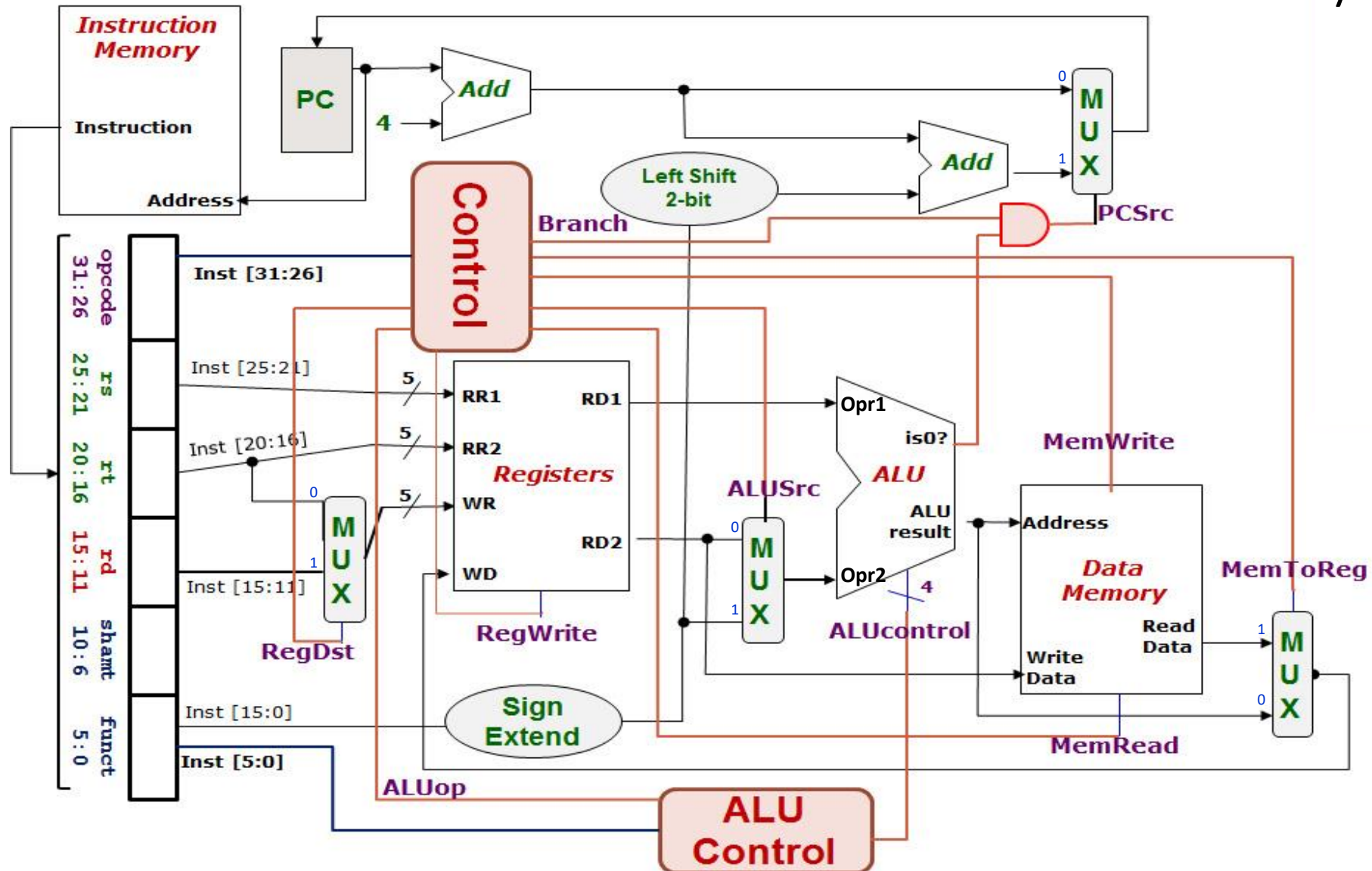

END OF FILE